

Laboratory job 23

Motor Reversing using Magnetic Starter

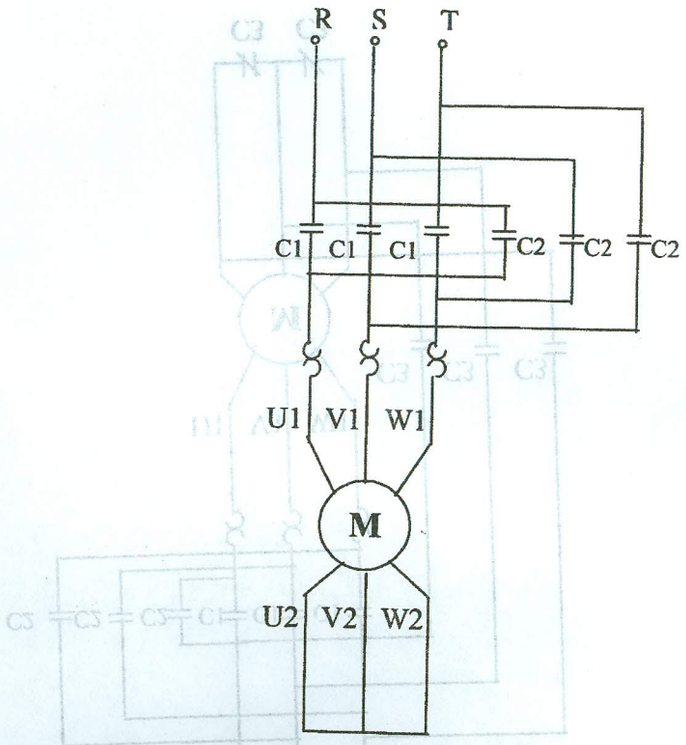

Power circuit

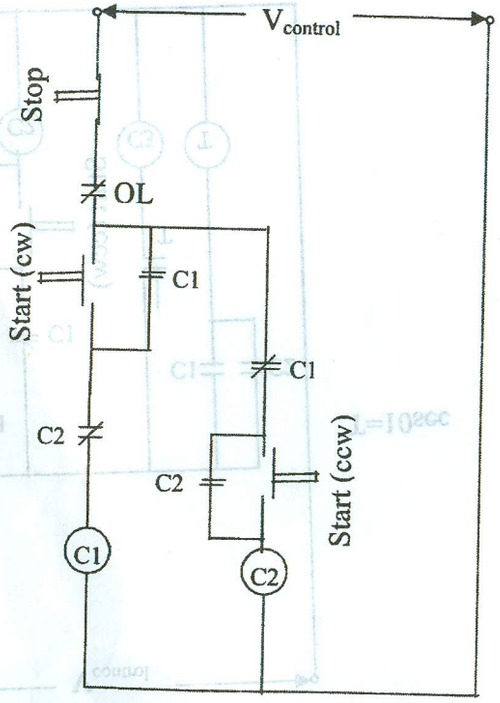

Control Circuit